

4X1 MULTIPLEXER:

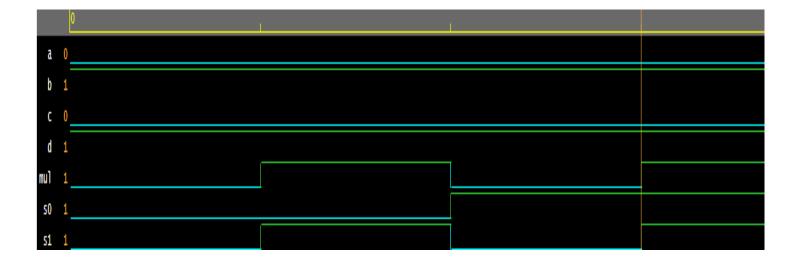


TERNARY OPERATOR:

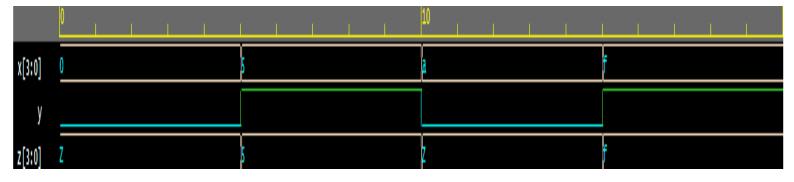

4 BIT UNIDIRECTIONAL BUS:



3X8 DECODER:

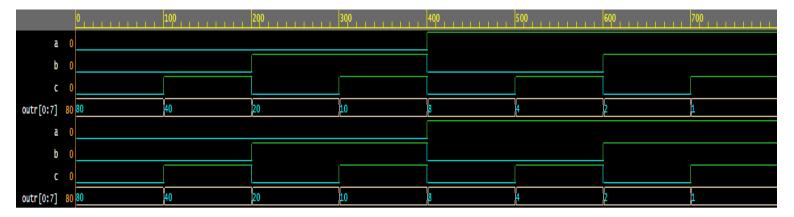

<u> 8X1 MULTIPLEXER:</u>

