

Name - MD Qusai Jawed
 Department - CSE (Second Year)
 Semester - 4th
 Roll No. - 37

Sub - Computer
 Architecture Lab

Date - 03.03.23

AND GATE :-



Truth Table :-

Input		Output
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

- When a logic simulator is selected, time slot not required in Ede.
- Error in default test bench & design: Can't create.

Code i) Design Module :-


```
module and2
(input A;
 input B;
 output C);
assign C = A & B;
end module
```

ii) Test Bench :-

```
timescale 1ns/10ps
module and2_tb;
reg A, B;
wire C;
and2 uut (.A(A), .B(B), .C(C));
initial
begin
A = 0;
B = 0;
#10;
A = 1;
B = 0;
#10;
A = 1;
B = 1;
#10;
end
end module
```

Name	Value	0 ns	500
A	1		
B	1		
C	1		

OR GATE :-

 

$$C = A + B$$

Truth Table :-

Input		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Code

i) Design Module :


```
module Or2
  (input A,
   input B,
   output C
  );
  assign C = A|B;
end module
```

Name	Value	0ns	500
A	1		
B	1		
C	1		

ii) Test Bench :

```
timescale 100ns
reg A, B;
wire C;
Or2 uut(.A(A), .B(B), .C(C));
initial
  begin
    A = 0;
    B = 0;
    #10;
    A = 0;
    B = 1;
    #10;
    A = 1;
    B = 0;
    #10;
    A = 1;
    B = 1;
    #10;
  end
end module
```

XOR GATE :-

 

$$C = A \oplus B$$

Truth Table :-

Input		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

Code :-

i) Design Module :-

```
module xor2
  (input A,
   input B,
   output C
  );
  assign C = A^B;
end module
```


Name	Value	0 ns	500
A	1		
B	1		
C	0		

ii) Test Bench :-

```
timescale 1ns/10ps
module xor2_tb;
  reg A, B;
  wire C;
  xor2 uut (.A(A), .B(B), .C(C));
  initial
    begin
      A = 0;
      B = 0;
      #10;
      A = 0;
      B = 1;
      #10;
      A = 1;
      B = 0;
      #10;
      A = 1;
      B = 1;
      #10;
    end
end module
```

NAND GATE :-

$$C = \overline{A \cdot B}$$

 

Truth Table :-

Input		Output
A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Code :-

i) Design module :-

```
module nand2
    (input A,
     input B,
     output C
    );
    assign C = ~(A & B);
end module
```

Name	Value	0 ns	1500
A	1		
B	1		
C	0		

ii) Test Bench :-

```
timescale 1ns/10ps
module nand2_tb;
    reg A, B;
    wire C;
    nand2 uut (.A(A), .B(B), .C(C));
    initial
        begin
            A = 0;
            B = 0;
            #10;
            A = 1;
            B = 0;
            #10;
            A = 0;
            B = 1;
            #10;
            A = 1;
            B = 1;
            #10;
        end
end module
```


NOR GATE :-



$$C = \overline{A+B}$$

Truth Table :-

Input		Output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Code :-

i) Design module :-


```
module nor2
    (input A,
     input B,
     output C
    );
    assign C = ~(A|B);
end module
```

ii) Test bench :-

```
timescale 1ns/10ps
module nor2_tb;
    reg A, B;
    wire C;
    nor2 uut (.A(A), .B(B), .C(C));
    initial
        begin
            A = 0;
            B = 0;
            #10;
            A = 0;
            B = 1;
            #10;
            A = 1;
            B = 0;
            #10;
            A = 1;
            B = 1;
            #10;
        end
end module
```

Name	Value	0ns	500
A	1		
B	1		
C	0		

NOT GATE :-

 

Truth Table :-

Input	Output
A	C
0	1
1	0

Code :-

i) Design module:-

```
module not2
  (input A,
   output C
  );
  assign C = !A;
end module
```


Name	Value	0ns	500
A	1		
C	0		

ii) Test Bench:-

```
timescale 1ns/10ps
module not2_tb;
  reg A;
  wire C;
  not2 uut (.A(A), .C(C));
  initial
  begin
    A = 0;
    #10;
    A = 1;
    #10;
  end
end module
```

XNOR GATE :-

$$Z = \overline{A \oplus B}$$

 

Truth Table :-

Input		Output
A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

Code :-

i) Design module :-

```
module xnor2 (  
    input a;  
    input b;  
    output z;  
);  
assign z = ~(a^b);  
end module
```

Name	Value	0 ns	500
A	1		
B	1		
C	1		

ii) Test Bench :-

```
module xnor2-testbench;  
    reg a, b;  
    wire z;  
    xnor2 uut (.a(a), .b(b), z(z));  
    initial  
    begin  
        a = 0;  
        b = 0;  
        #100;  
        a = 0;  
        b = 1;  
        #100;  
        a = 1;  
        b = 0;  
        #100;  
        a = 1;  
        b = 1;  
        #100;  
    end  
    initial  
    begin  
        $dumpfile("dump.vcd");  
        $dumpvars();  
    end  
end module
```